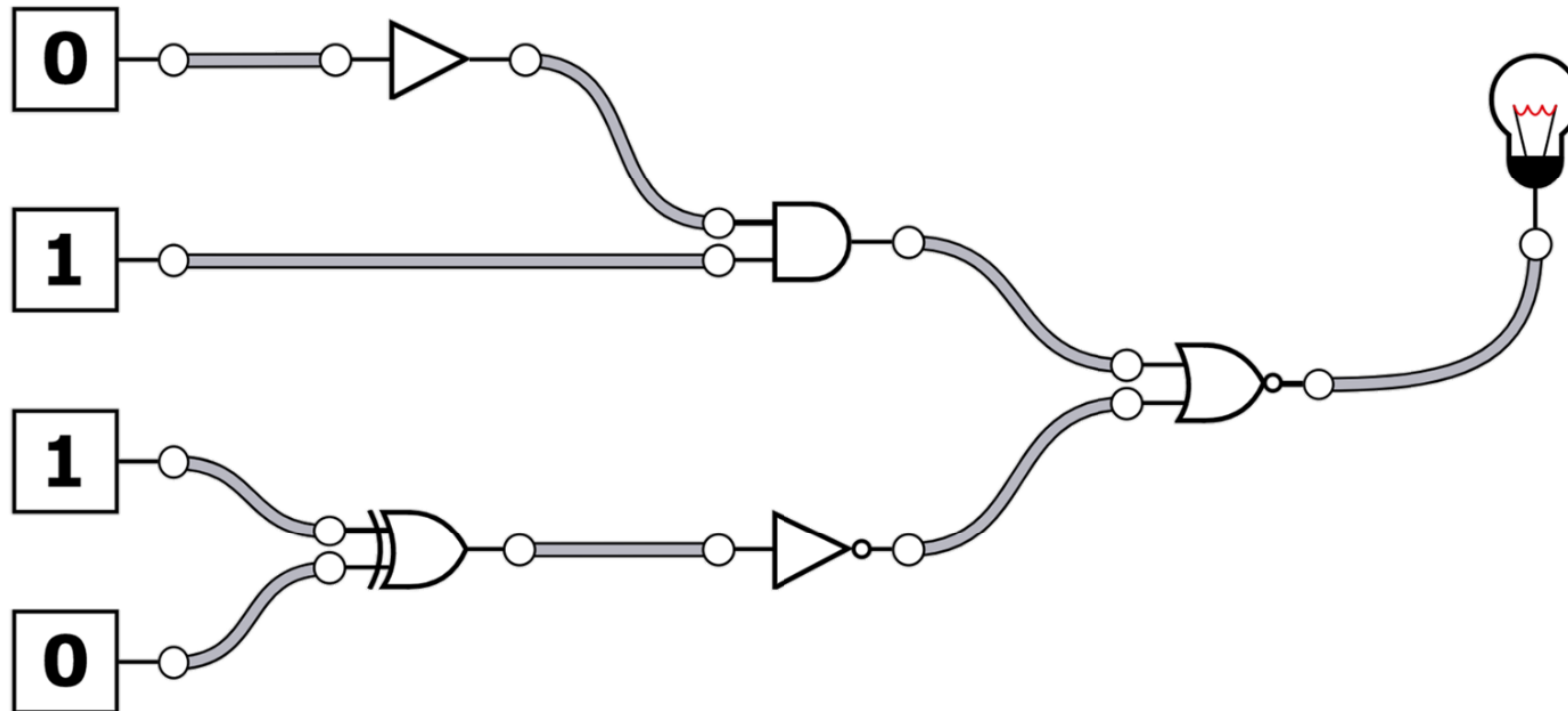




# CyberFirst Empower Cyber Week

## Logic Gate Challenge

Determine the outputs of each gate and decide if the lightbulb will light up (1 = ON, 0 = OFF)



*Tip: Take a look at our cheat sheet to help you!*