CyberFirst Empower Cyber Week

Logic Gate Challenge

Determine the outputs of each gate and decide if the lightbulb will light up (1 = ON, 0 = OFF)

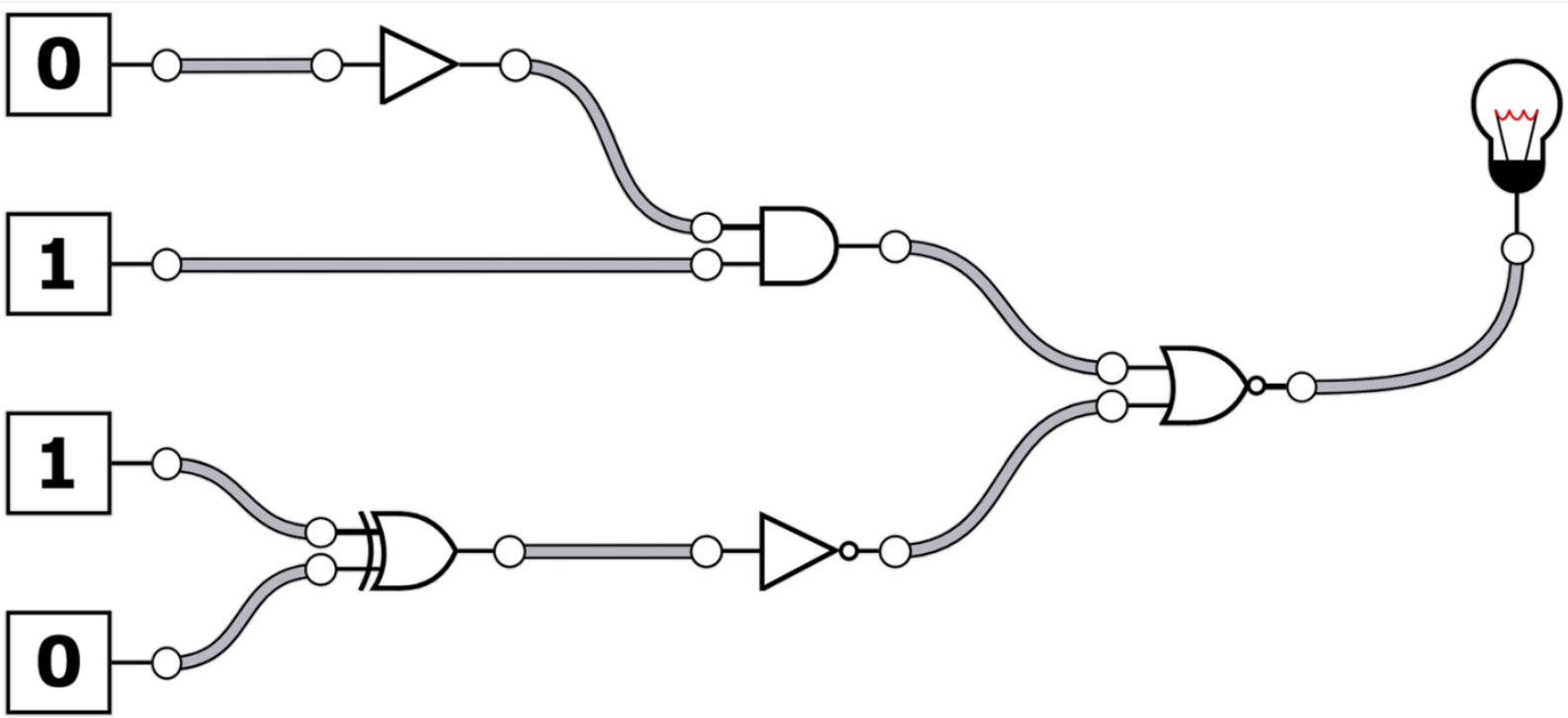

Tip: Take a look at our cheat sheet to help you!

This information is exempt under the Freedom of Information Act 2000 (FOIA) and may be exempt under other UK information legislation. Refer any FOIA queries to ncscinfoleg@ncsc.gov.uk. All material is UK Crown Copyright ©